 



# **High-Speed Serial Interface Circuits and Systems**

## **Design Exercise 8 – Continuous-Time Linear Equalizer (CTLE)**

# Continuous-Time Linear Equalizer(CTLE)



<Frequency response flattening>


 


<Integrated power spectrum of NRZ data>

● Until what frequency..??

- Nyquist frequency:  
In order to recover data,  
it is necessary to have bandwidth at least half of data rate  
ex) 2Gbps → 1GHz 3-dB bandwidth required


# Channel Characteristic

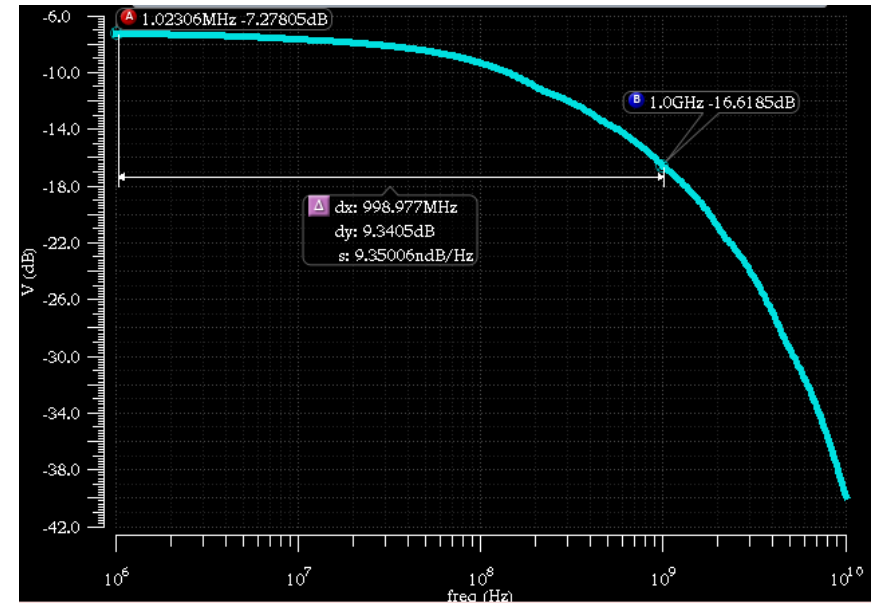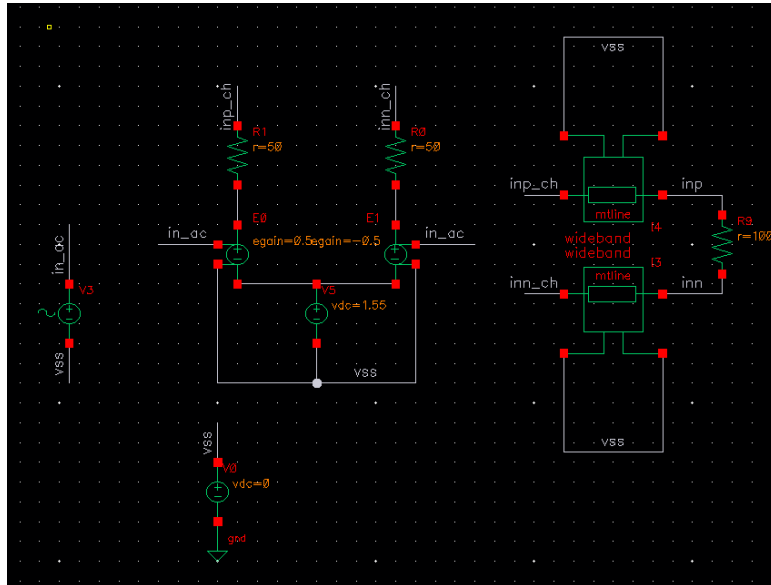

- mtline (microstrip)
  - Dielectric const.: 4.8
  - Dielectric layer thickness: 360u (m)
  - Signal line width: 625u (m)
  - Signal line thickness: 17.78u (m)
  - Physical length: 8 (m)

- Channel characteristics
  - DC loss = - 7.2 dB (Termination loss + @)
  - High freq. loss relative to DC @ 1 GHz = - 9.3 dB
- At least 6.3dB of boost at 1 GHz required to satisfy the Nyquist frequency

# Passive CTLE

 

$$H(s) = \frac{R_L}{R_s + R_L} \frac{sR_s C_s + 1}{s(R_s \parallel R_L)(C_s + C_L) + 1}$$


$$\text{Zero} = \frac{1}{R_s C_s}$$

$$\text{Pole} = \frac{1}{(R_s \parallel R_L)(C_s + C_L)}$$

$$\text{Peaking gain} = \left(1 + \frac{R_s}{R_L}\right) \left(\frac{C_s}{C_L + C_s}\right)$$

- Goal: Boost at least 6.3dB @ 1GHz  
→ Equalize 2Gbps data transmission
- 1 pole, 1 zero filter → HPF

# Passive CTLE AC Simulation

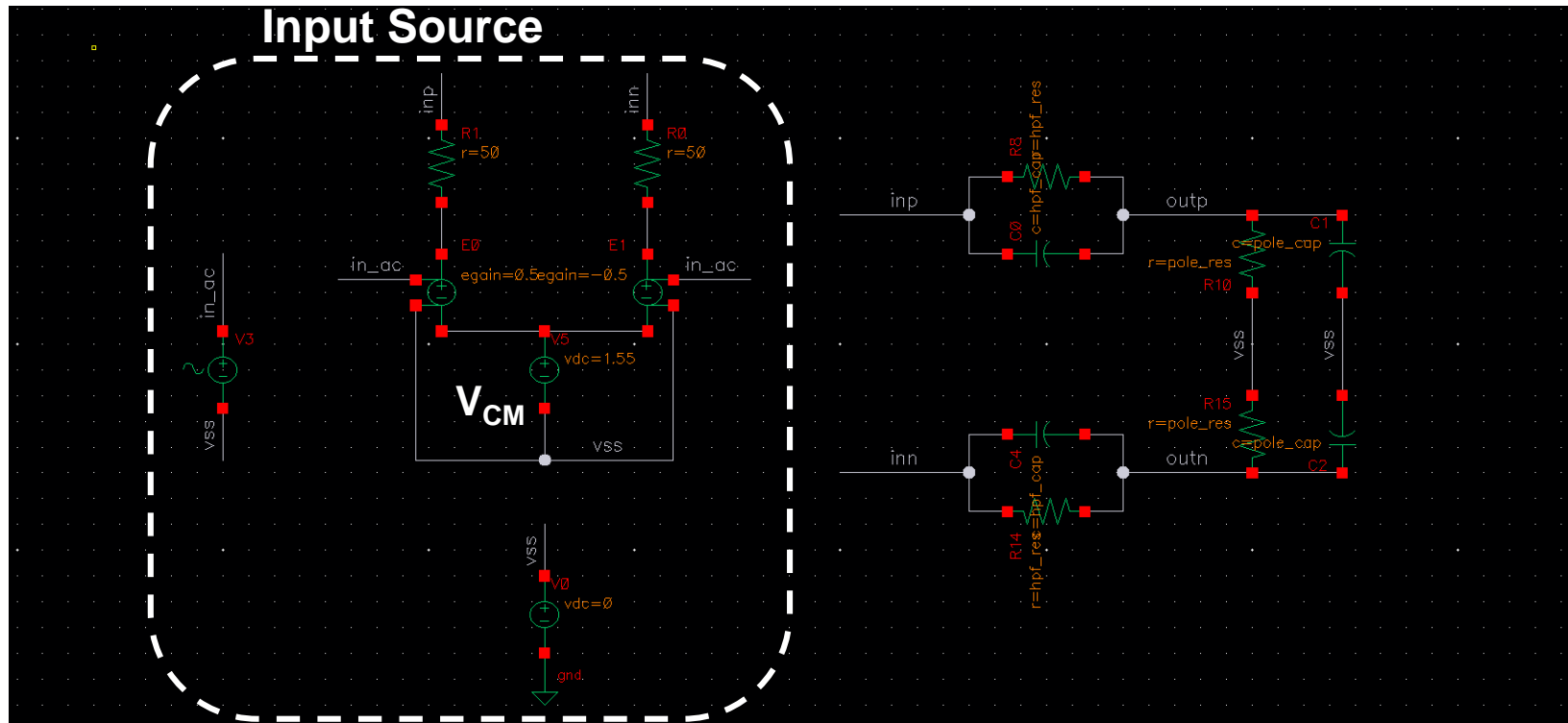



## Input source

- vcvs gain:  $\pm 0.5$
- $V_{CM}$ : 1.55V
- Input resistor: 50 Ohm
- Vsin: 1V ac magnitude

## Passive elements

- $R_S$ : 1 K $\Omega$
- $C_S$ : 800 fF
- $R_L$ : 500  $\Omega$
- $C_L$ : 50 fF


# Simulation Results

 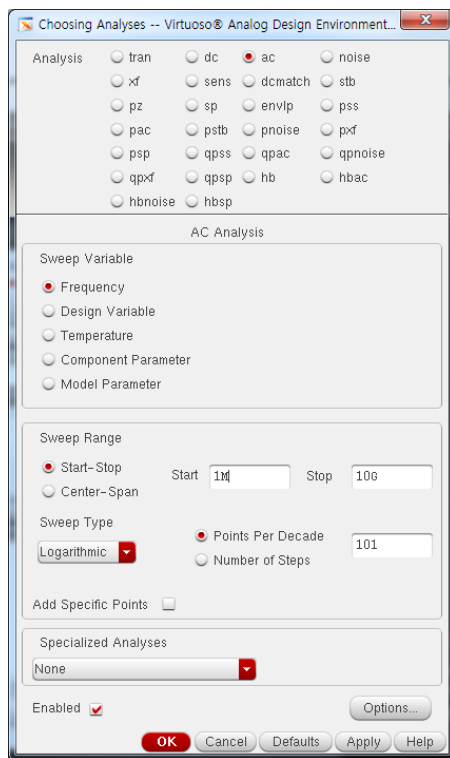


- 1M~10G, logarithmic, 101points
- DC loss : -9.8 dB
- 7.6dB peaking @ 1 GHz (Nyquist frequency)

# Simulation setup


## Transmitter (Source)

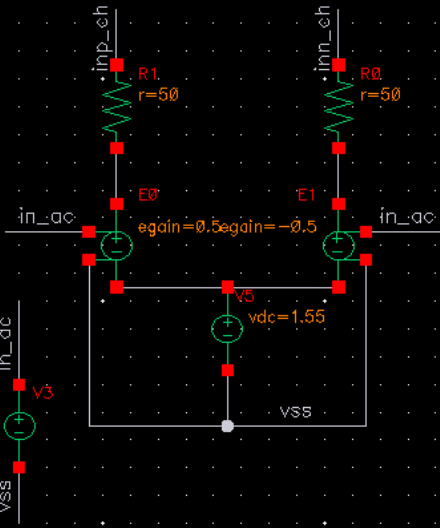


## FR4 Channel

 

## Passive CTLE

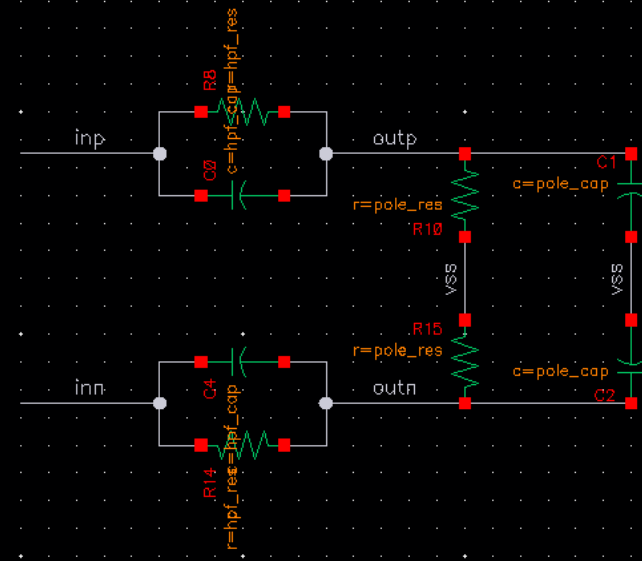



# Simulation Results (w/o EQ)

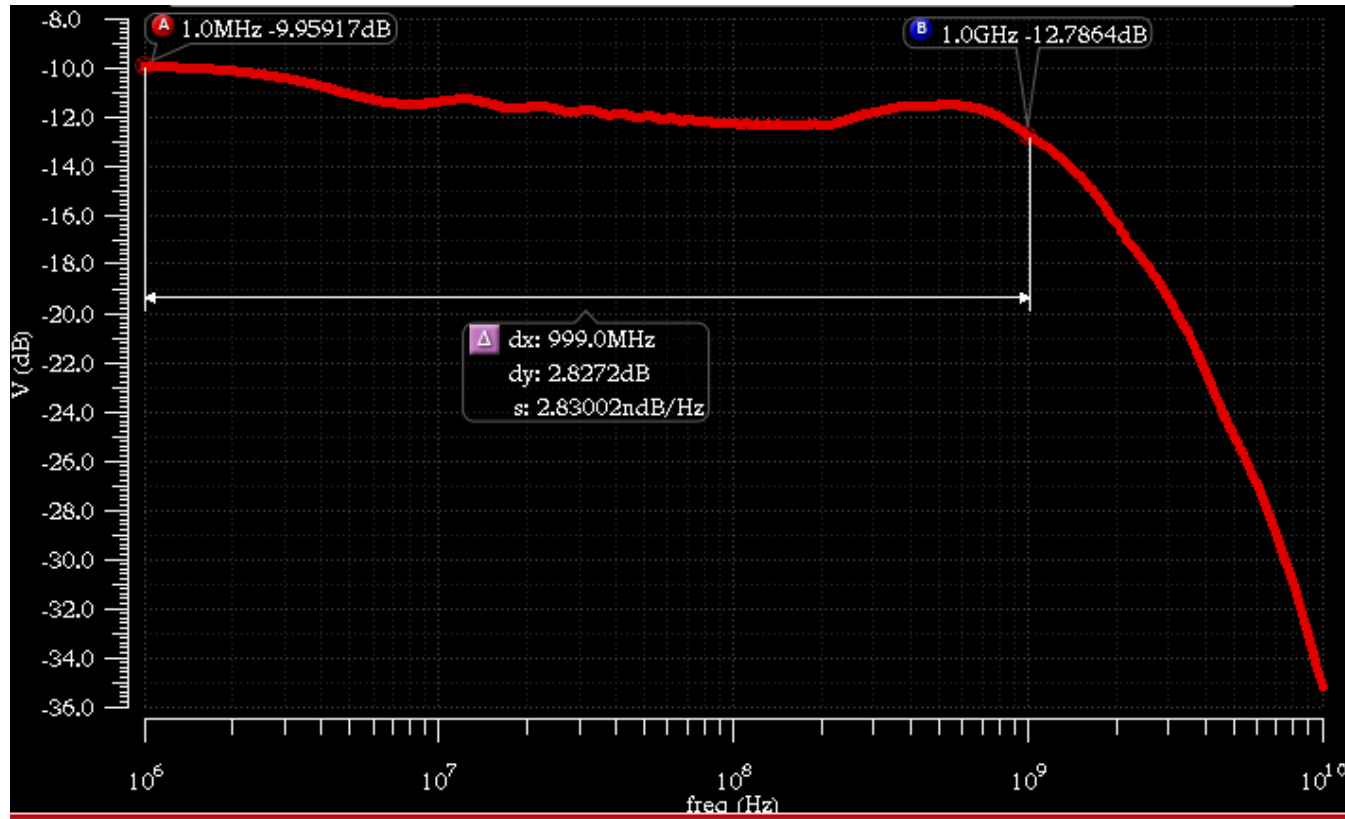

- Expected compensated channel loss @ 1 GHz =  $-9.3 + 7.6 = -1.7$  dB
- Simulated compensated channel loss @ 1 GHz =  $-2.8$  dB ???




# Passive EQ impedance problem

  


- Input impedance is not well matched!
- To alleviate this problem, additional matching component is needed.
- In practical design, each passive element must be carefully set for impedance matching.

# Modified simulation setup


## Transmitter (Source)

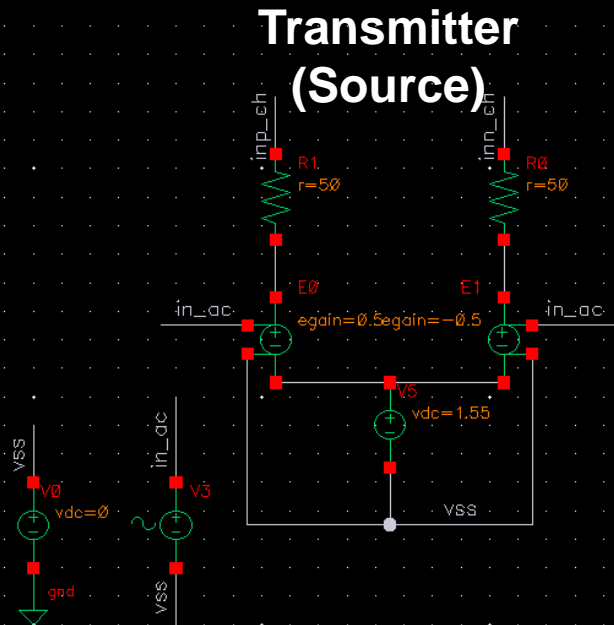

## FR4 Channel

 


## Passive CTLE

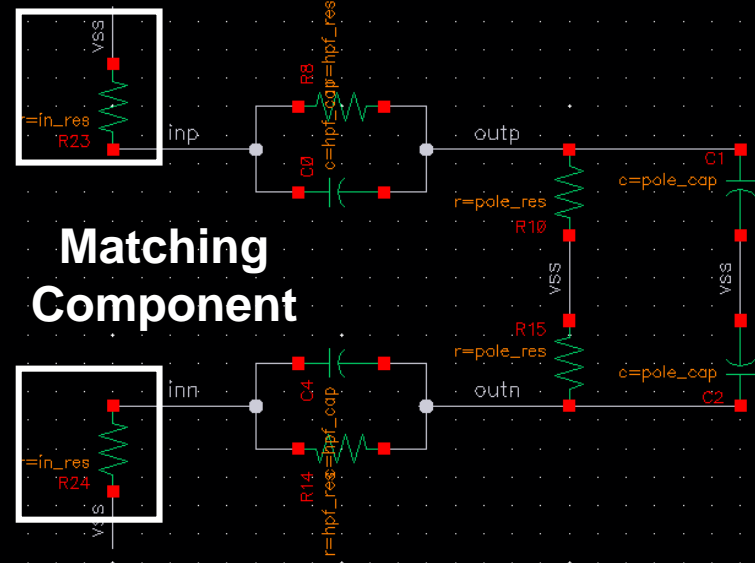


## Matching Component

# Simulation Results (w/o EQ)

 

- DC loss =  $-6 - 1.2 = -7.2$  dB
- Channel loss @ 1 GHz =  $-9.3$  dB


# Simulation Results (w/ EQ)

 

● DC loss =  $-6 - 1.2 - 9.8 = -17$  dB

● Channel loss @ 1 GHz =  $-9.3 + 7.6 + @ = -1.5$  dB


# Active CTLE – Source Degeneration

 


$$H(s) = \frac{g_m}{C_p} \frac{\overbrace{s + \frac{1}{R_S C_S}}^{\text{1st zero}}}{\underbrace{\left(s + \frac{1 + \frac{g_m R_S}{2}}{R_S C_S}\right)}_{\text{1st pole}} \underbrace{\left(s + \frac{1}{R_D C_p}\right)}_{\text{2nd pole}}}$$

$$\text{Peaking gain} = 1 + \frac{g_m R_S}{2}$$

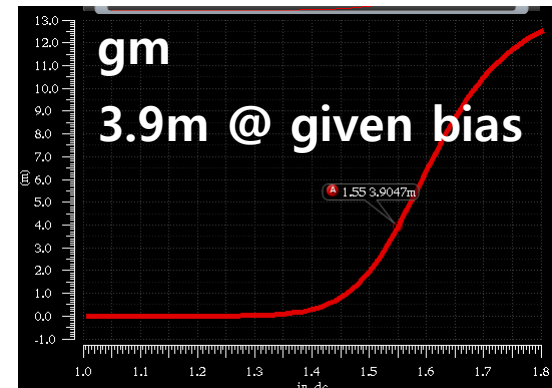- Goal: Boost at least 6.3dB @ 1GHz  
→ Equalize 2Gbps data transmission
- 2 pole, 1 zero change with R,C tuning





# Active CTLE AC Simulation

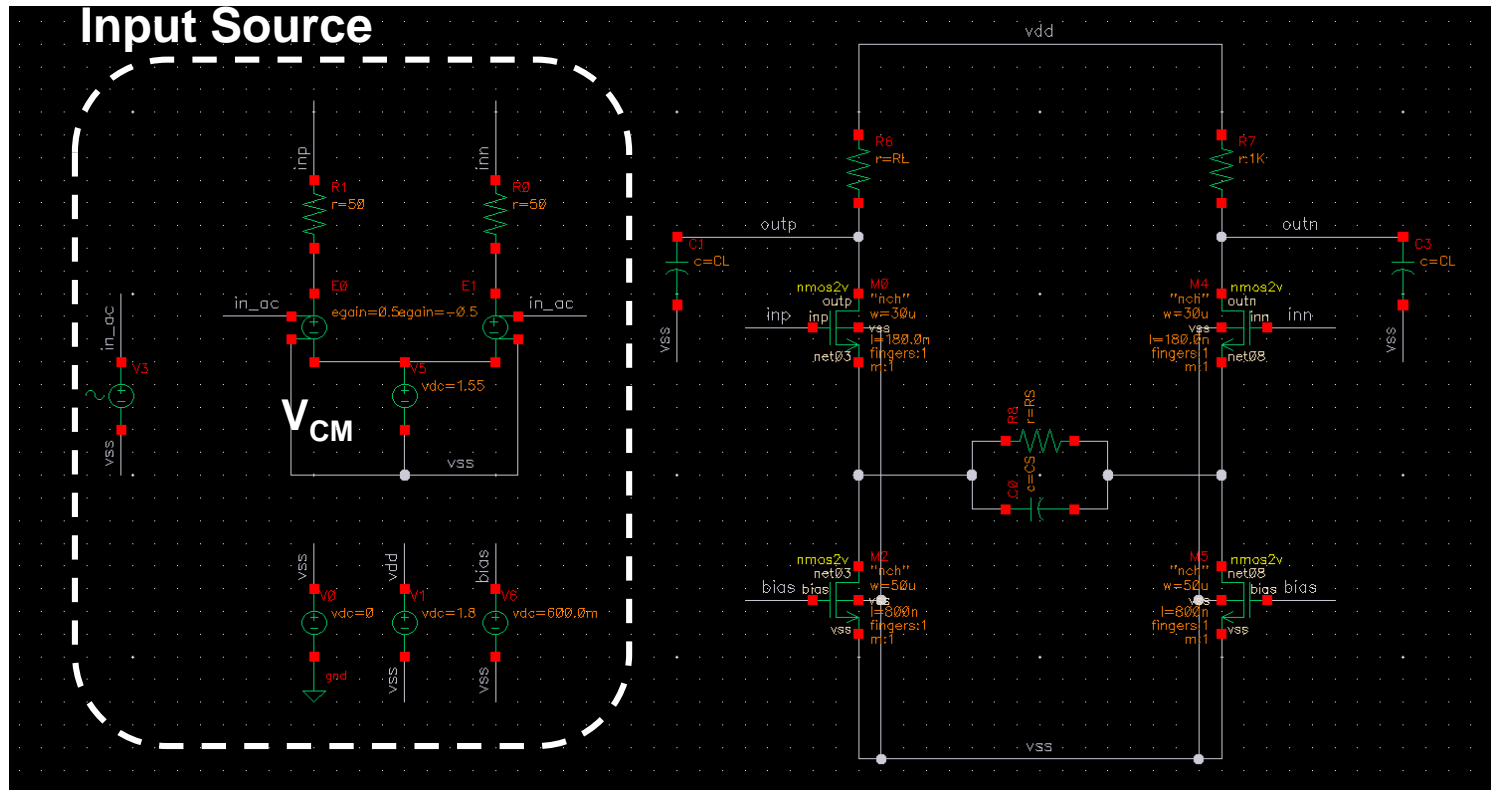

- Input source
  - vcvs gain:  $\pm 0.5$
  - $V_{CM}$ : 1.55V
  - Input resistor: 50 Ohm
  - Vsin: 1V ac magnitude
- CTLE
  - Input MOSFETs: 30u/180n
  - Tail MOSFETs: 50u/800n
  - Load resistors: 1 K $\Omega$
  - Load capacitor: 50 fF
- Degeneration Filter
  - $R_{deg}$ : 1 k $\Omega$
  - $C_{deg}$ : 800 fF
  - Tail MOSFET bias: 0.6 V


# Simulation Results

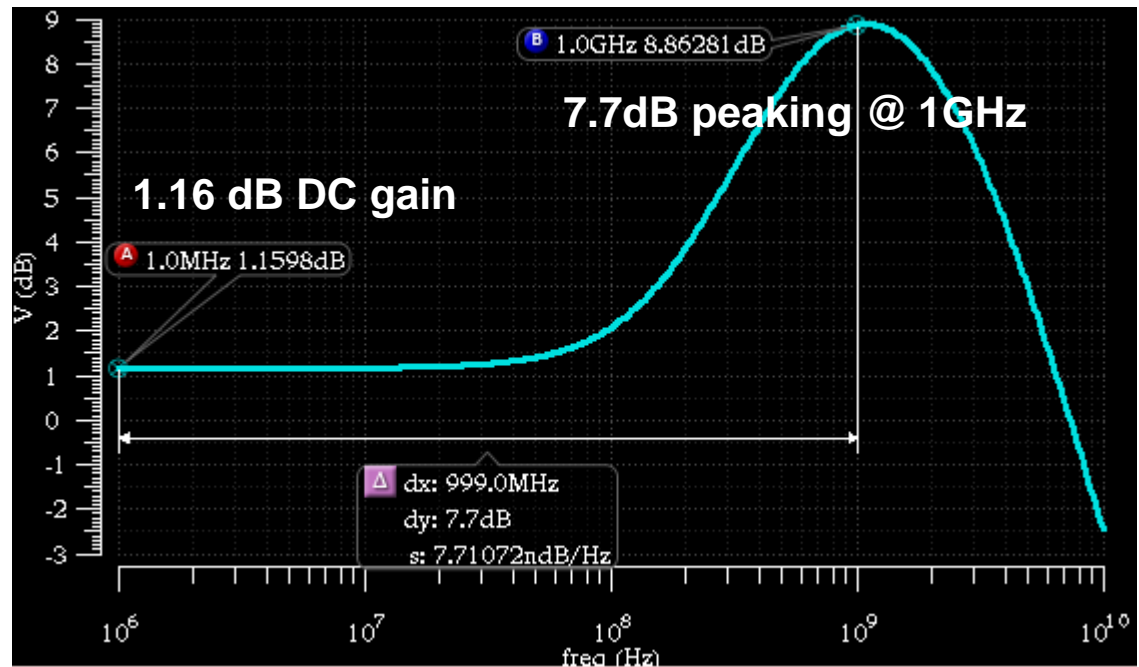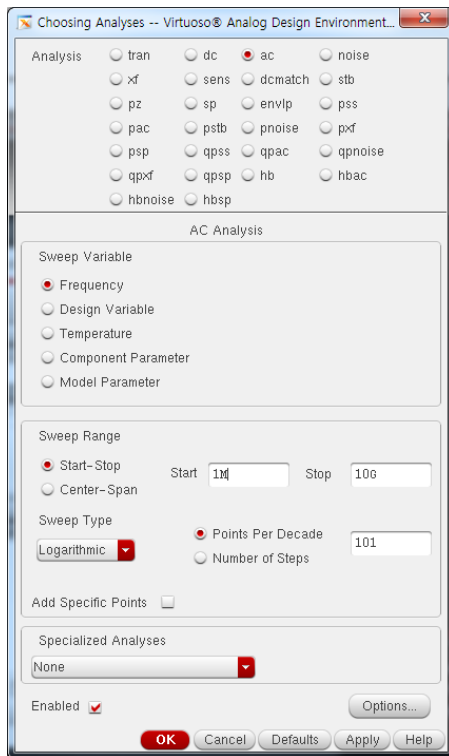


- 1M~10G, logarithmic, 101points
- DC gain : 1.1 dB
- 7.7dB peaking @ 1 GHz (Nyquist frequency)

# Channel + CTLE AC Simulation


## Transmitter (Source)

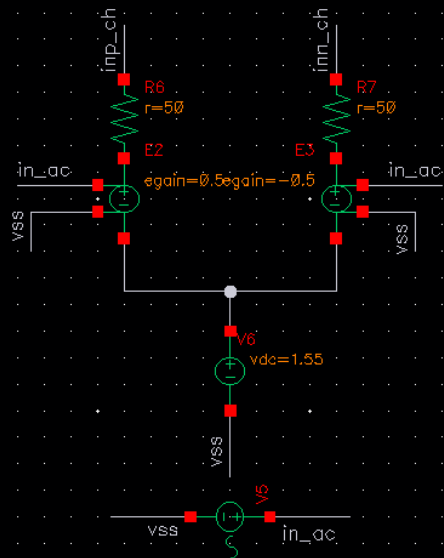

## 8-m FR4 Channel

 


## Active CTLE

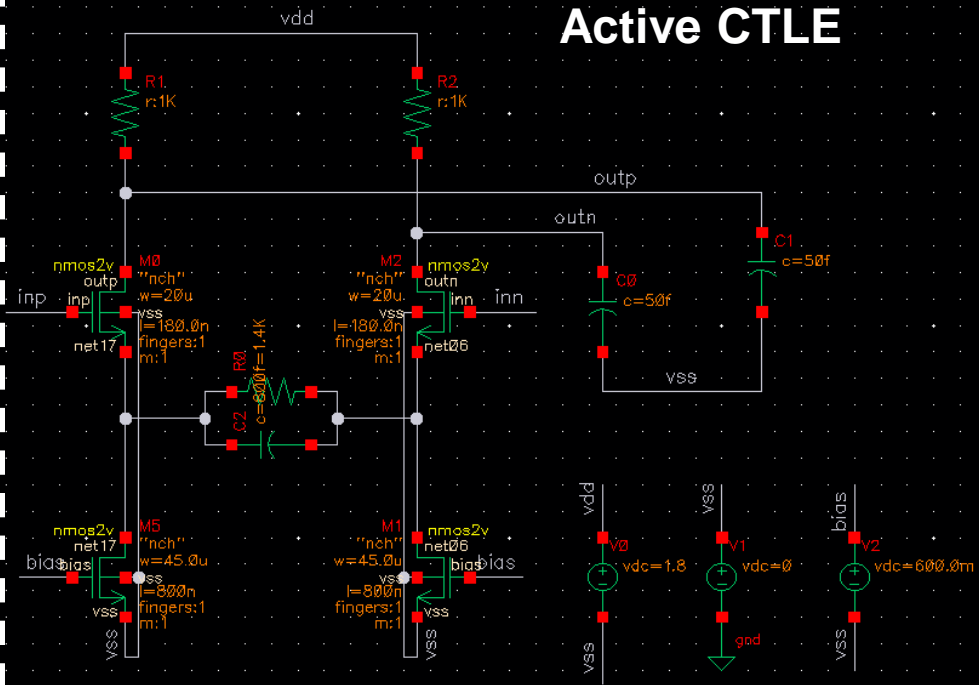




# Simulation Results (w/o EQ)

 



- DC loss =  $-6 - 1.2 = -7.2$  dB
- Channel loss @ 1 GHz =  $-9.3$  dB

# Simulation Results(Channel + CTLE)

 

- DC loss =  $-6 - 1.2 + 1.1 = -6.1$  dB
- Channel loss @ 1 GHz =  $-9.3 + 7.7 = -1.6$  dB

# Channel + CTLE Transient Simulation

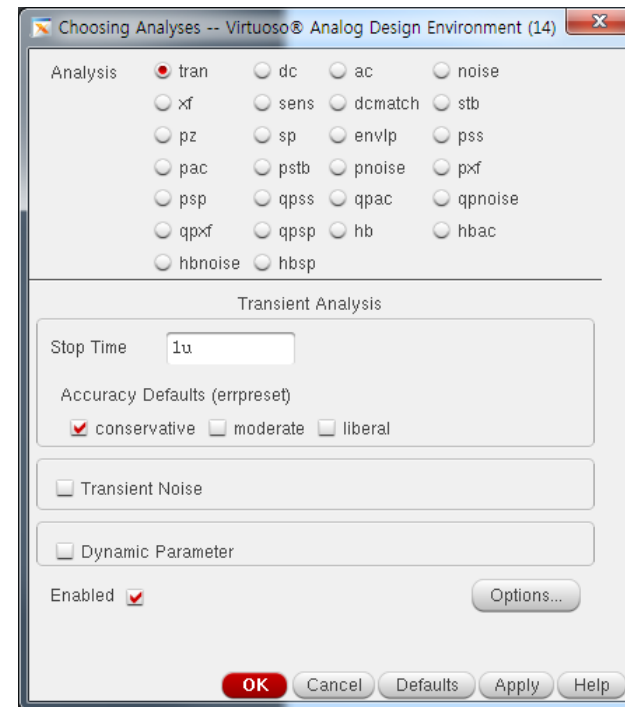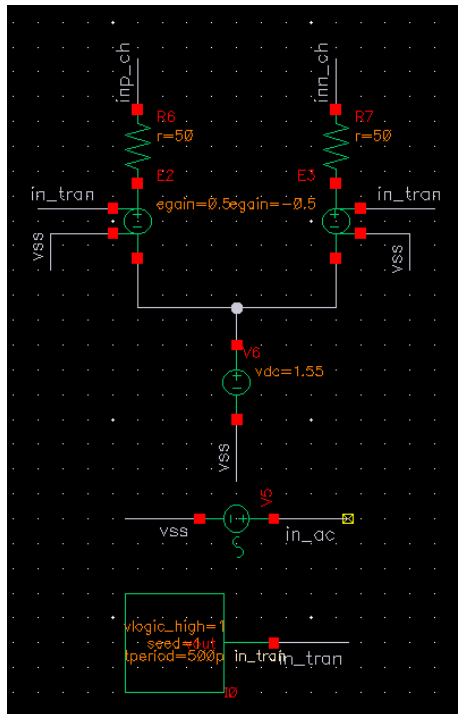


## Random bit stream


- Period:  $1/2\text{Gbps} = 500\text{ps}$
- seed: 1
- vlogic\_high, low = 1, -1  $\rightarrow$  500mV swing to Rx
- trise, tfall = 20p

# Simulation Results(Channel + CTLE)

- Passive CTLE

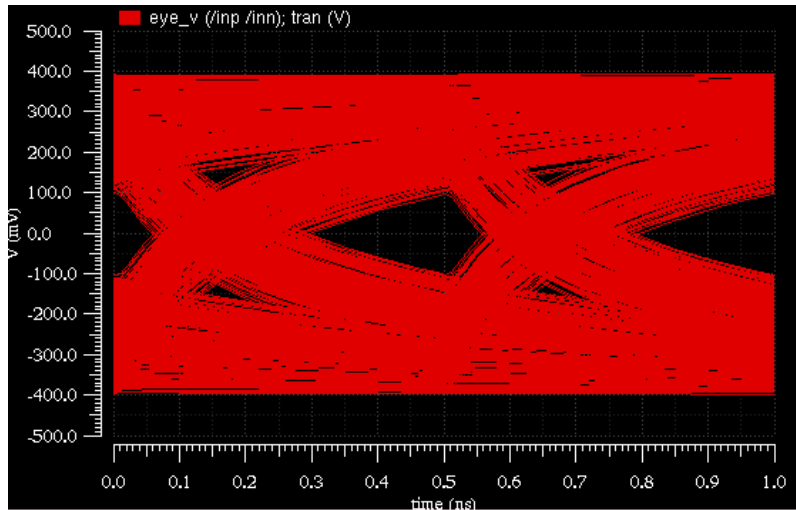


<Before EQ>

 


<After EQ>

# Simulation Results(Channel + CTLE)

- Active CTLE – Source degeneration

 


<Before EQ>

 


<After EQ>

# SNR Calculation

 


- Calculate the center of your eye diagram. (In this picture,  $(75p+575p)/2 = 325p$ )
- x-range is  $\pm 10\%$  (100ps) from the center of the eye. (In this picture,  $x\text{-range} = 225p \sim 425p$ )

# SNR Calculation

 

< Passive CTLE >

 - Eye level is degraded. (DC loss!)
- No power consumption



< Active CTLE >

- Eye level is not degraded. (by active components)
- Power consumption is needed.

# Homework

## Rx CTLE

For the channel used today, design a passive and active CTLE that can recover 3 Gb/s data.

- Attach the passive component value, frequency response, and transient simulation results.